

23 April 2007

Create a clock-synchronous VHDL entity with a 4-bits control input (**CTL4**) and a parallel 12-bits output (**OUT12**).

Starting from a reset, the entity must sample the input **CTL4** and receive data from a serial input (**DATAIN**). If the first 4 bits from the serial input stream are equal to the control word sampled from **CTL4**, the entity must transfer these 4 bits to the output followed by the subsequent 8 bits from **DATAIN**. The entity must set the output to high impedance in any other situation and when the enable signal is set to 0.

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_ARITH.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6
7  entity Key_Rec is
8      port(CLK, DATAIN, ENABLE, RESET: in std_logic;
9           CTL4: in std_logic_vector (3 downto 0);
10          OUT12: out std_logic_vector(11 downto 0) );
11 end Key_Rec;
12
13
14 architecture Behavioral of Key_Rec is
15
16     signal key: std_logic_vector (3 downto 0); --For sampling the key word in CTL4.
17     signal reg: std_logic_vector (11 downto 0); --For uploading the input DATAIN.
18     signal cnt: integer range 0 to 15:=0;
19
20     begin
21
22         process (CLK, RESET)
23
24             begin
25
26                 if (RESET='1') then
27                     --If a reset pulse occurs, a general reset is executed:
28                     reg <= (others => '0');
29                     out12 <= (others => '0');
30                     key <= (others => '0');
31                     cnt <= 0;
32                 elsif (rising_edge (CLK)) then
33                     if(cnt < 12) then
34                         reg <= reg(10 downto 0) & DATAIN;
35
36                         --At the beginning of the upload (cnt=0), control input is sampled;
37                         --for the remaining values from DATAIN, just the increment of cnt is executed
38                         case cnt is
39                             when 0 => key <= CTL4;
40                                 cnt <= cnt + 1;
41
42                             when 1 to 12 => cnt <= cnt + 1;
43
44                             --No action is required in this case.
45                             when others => null;
46                         end case;
47                     end if;
48
49                     --After the upload is complete, the output is computed:
50                     --if the output is enabled and the first four bits
51                     --of DATAIN are equal to the control input, the serial input is sent to parallel
52                     --output; otherwise, the output is set to high impedance.
53                     if ((cnt >= 12) and (ENABLE = '1') and (reg (11 downto 8) = key)) then
54                         out12 <= reg;
55                     else
56                         out12 <= (others => 'Z');
57                     end if;
58                 end if;
59             end process;
60
61         end process;
62
63     end Behavioral;
64
```

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.STD_LOGIC_ARITH.ALL;
USE IEEE.STD_LOGIC_UNSIGNED.ALL;

ENTITY key_recognizer IS
PORT (
        CLK, ENABLE, RESET: IN std_logic;           -- INGRESSI DI CONTROLLO
        DATAIN: IN std_logic;                       -- DATI IN INGRESSO
        CTL4 : IN std_logic_vector(3 downto 0);      -- PAROLA CHIAVE
        OUT12 : OUT std_logic_vector(11 downto 0)    -- DATI IN USCITA
    );
END key_recognizer;

architecture Behavioral of key_recognizer IS
    signal CONT: integer range 0 to 15:=15;          -- segnale di conteggio
    signal data_reg:std_logic_vector(11 downto 0);   -- registro per appoggiare i dati
    signal key_reg:std_logic_vector(3 downto 0);     -- registro per la parola chiave

begin
    process(CLK,RESET) -- il processo è attivato dal clock e dal reset asincrono
    begin
        if(RESET='1') then
            key_reg <= (others=>'0');                -- azzeriamo il contenuto dei registri
            data_reg<=(others=>'0');
            CONT <=0;                                -- azzeriamo il contatore
        elsif(CLK'event and CLK='1') then
            data_reg<=data_reg(10 downto 0) & DATAIN; -- i dati entrano nel registro
            -- il conteggio si incrementa fino a 13 e poi si ferma
            -- inoltre quando è 0 campioniamo pure l'ingresso CTL4
            case CONT is
                when 0      =>    CONT <= CONT + 1;
                                key_reg <= CTL4;
                when 1 to 12 =>    CONT <= CONT + 1;
                when others =>    null;
            end case;
        end if;
    end process;

    -- a questo punto non resta che copiare il data_reg all'uscita OUT12
    -- nelle condizioni di conteggio a 12, di abilitazione attiva
    -- e di soddisfacimento della parola chiave
    OUT12 <= data_reg
    when ((data_reg(11 downto 8)=key_reg) and ENABLE='1' and CONT=12)
    else "ZZZZZZZZZZZZ";
end Behavioral;

```