

25 June 2013

Create a clock-synchronous VHDL entity which implements a vertical and horizontal parity generator.

Starting from a **LOAD** pulse, the entity must read four 4-bits words from the input **DATAIN** and a control signal **PARITY** which determines whether the parity is even or odd.

The entity must produce a serial output **DATAOUT** containing the input values and the computed parity values, properly collocated in time.

Example:


#	DATI IN INGRESSO				PL
1	0	0	1	1	1
2	1	1	1	1	1
3	0	0	0	1	0
4	0	1	0	1	1
PT	0	1	1	1	0

PL = Horizontal parity

PT = Vertical parity

DATI IN INGRESSO = Input Data

 The entity must check the flow of input to avoid data accumulation inside the entity and emit output data in the shortest time possible.



```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_ARITH.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6
7  entity Parity_Gen is
8      port(CLK, LOAD, parity: in std_logic;
9           DATAIN: in std_logic_vector (3 downto 0);
10          DATAOUT: out std_logic);
11 end Parity_Gen;
12
13
14 architecture Behavioral of Parity_Gen is
15
16     --regOut must contain 4 words of 4 bits, 4 trasverse parity bits,
17     --4 longitudinal parity bits and one trasverse and longitudinal bit.
18     signal regOut: std_logic_vector (24 downto 0):=(others => 'Z');
19     signal cnt: integer range 0 to 35:=0;
20
21     --to store parity input
22     signal p: std_logic;
23
24     begin
25
26     process (CLK, LOAD)
27     begin
28         if (LOAD = '0') then
29             DATAOUT <= 'Z';
30             cnt <= 0;
31         elsif rising_edge(CLK) then
32             if (cnt < 31) then
33                 --Parity bit is computed as follows: the exclusive or (XOR) of the 4 bits of
34                 --DATAIN tells if the number of ones is even (0) or odd (1);
35                 --the XOR of this result and parity input gives the correct longitudinal
36                 --parity input for each DATAIN.
37
38                 --At the beginning, parity input is stored so that the same value (the first one
39                 --after LOAD becomes '1') is used during the output processing.
40                 --NOTE: Parity bit cannot be processed right after the assignment because the
41                 --present value of every signal is used during the process execution and the
42                 --new values are assigned once the process is ended. So the parity bit, for each
43                 --case, must be processed in the next case:
44                 case cnt is
45                     when 0 => p <= parity;
46                             regOut(24 downto 21) <= DATAIN;
47                             DATAOUT <= 'Z';
48                             cnt <= cnt + 1;
49
50                     when 1 => regOut(19 downto 16) <= DATAIN;
51
52                             regOut(20) <= regOut(24) xor regOut(23) xor
53                             regOut(22) xor regOut(21) xor p;
54
55                             DATAOUT <= 'Z';
56                             cnt <= cnt + 1;
57
58                     when 2 => regOut(14 downto 11) <= DATAIN;
59
60                             regOut (15) <= regOut(19) xor regOut(18) xor
61                             regOut(17) xor regOut(16) xor p;
62
63                             DATAOUT <= 'Z';
64                             cnt <= cnt + 1;
65
66                     when 3 => regOut(9 downto 6) <= DATAIN;
67
68                             regOut (10) <= regOut(14) xor regOut(13) xor
69                             regOut(12) xor regOut(11) xor p;
70
71                             DATAOUT <= 'Z';
72                             cnt <= cnt + 1;
73
74
75
76
```

```
77
78     --Trasverse parity bits must be processed after the whole input data is stored
79     --for sure; in this context also the last longitudinal parity bit is processed.
80     when 4 => regOut(5) <= regOut(9) xor regOut(8) xor
81                   regOut(7) xor regOut(6) xor p;
82
83         regOut(4) <= regOut(24) xor regOut(19) xor
84                   regOut(14) xor regOut(9) xor p;
85
86         regOut(3) <= regOut(23) xor regOut(18) xor
87                   regOut(13) xor regOut(8) xor p;
88
89         regOut(2) <= regOut(22) xor regOut(17) xor
90                   regOut(12) xor regOut(7) xor p;
91
92         regOut(1) <= regOut(21) xor regOut(16) xor
93                   regOut(11) xor regOut(6) xor p;
94
95         cnt <= cnt + 1;
96         DATAOUT <= 'Z';
97
98     --When every longitudinal parity bit is processed, the last trasverse parity bit
99     --can be processed as well
100    when 5 => regOut(0) <= regOut(4) xor regOut(3) xor regOut(2) xor regOut(1) xor p;
101            cnt <= cnt + 1;
102            DATAOUT <= 'Z';
103
104    --Output processing: the MSB of regOut is sent to serial output and then all of
105    --the values of regOut are shifted to the left and the LSB is replaced by 'Z':
106    when 6 to 31 => DATAOUT <= regOut(24);
107                    regOut <= regOut(23 downto 0) & 'Z';
108                    cnt <= cnt + 1;
109    when others => null;
110
111    end case;
112
113    --After the output processing is finished, the output bitstream is set to high impedance
114    elsif (cnt >= 31) then
115        DATAOUT <= 'Z';
116    end if;
117
118    end if;
119
120    end process;
121
122    end Behavioral;
123
```

```

1  -- Possibile Soluzione della Prova del 25 Giugno 2013      -   Giaconia      --
2  -- La codifica si basa sulla presenza di un contatore ed un registro a 25 bit che --
3  -- ospita i dati in ingresso. L'entità nei primi 5 clock a partire dall'impulso Load --
4  -- carica il registro con i dati e calcola tramite xor i bit di parità; poi fa uno --
5  -- shift a sinistra del registro e mette in uscita il registro stesso. La macchina --
6  -- riparte quando vi è un nuovo impulso di load azzerando il contatore e campionando --
7  -- nuovamente il segnale di parità da usare --
8
9  library IEEE; use IEEE.STD_LOGIC_1164.ALL;
10 use IEEE.STD_LOGIC_ARITH.ALL; use IEEE.STD_LOGIC_UNSIGNED.ALL;
11
12 entity parity_check is
13     port(clk, load, parity: in std_logic; din: in std_logic_vector(3 downto 0);
14           dout: out std_logic);
15 end parity_check;
16
17 architecture Behavioral of parity_check is
18     signal regpar:std_logic:='0'; signal cnt: integer :=0; -- segnali per parità ed il conteggio
19     signal vett: std_logic_vector(24 downto 0):=(others =>'Z');
20 begin
21     process(clk)
22     begin
23         if load = '1' then
24             cnt<=0; regpar<=parity; -- qui azzero il conteggio e registro la parità
25         elsif clk'event and clk = '1' then -- da usare
26             if cnt<=31 then cnt<=cnt+1; end if; -- il contatore cadenza 32 stati (da 0 a 31)
27
28             case cnt is
29                 when 0 => vett(24 downto 21) <= din; -- carico il primo dato
30                 when 1 => vett(19 downto 16) <= din; -- carico il secondo dato
31                     -- calcolo la parità del primo con i dati al passo precedente
32                     vett(20) <= vett(24) xor vett(23) xor vett(22) xor vett(21) xor regpar;
33                 when 2 => vett(14 downto 11) <= din; -- carico il terzo dato
34                     vett(15) <= vett(19) xor vett(18) xor vett(17) xor vett(16) xor regpar;
35                 when 3 => vett(9 downto 6) <= din; -- carico il quarto dato
36                     vett(10) <= vett(14) xor vett(13) xor vett(12) xor vett(11) xor regpar;
37                     -- calcolo la parità del quarto dato
38                 when 4 => vett(5) <= vett(9) xor vett(8) xor vett(7) xor vett(6) xor regpar;
39                     -- calcolo i 4 bit per la parità trasversale
40                     vett(4) <= vett(24) xor vett(19) xor vett(14) xor vett(9) xor regpar;
41                     vett(3) <= vett(23) xor vett(18) xor vett(13) xor vett(8) xor regpar;
42                     vett(2) <= vett(22) xor vett(17) xor vett(12) xor vett(7) xor regpar;
43                     vett(1) <= vett(21) xor vett(16) xor vett(11) xor vett(6) xor regpar;
44                     -- calcolo la parità longitudinale del dato di par. trasversale
45                 when 5 => vett(0) <= vett(20) xor vett(15) xor vett(10) xor vett(5) xor regpar;
46                     -- faccio lo shift a sinistra dei dati ed emetto in uscita
47                 when 6 to 31 => vett <= vett(23 downto 0) & 'Z';
48                     dout <=vett(24);
49                 when others => null;
50             end case;
51         end if;
52     end process;
53 end Behavioral;
54

```