

20 June 2008

Create a VHDL entity to implement a chronometer with tenth of a second precision.


The format is mm:ss:d – The chronometer will be able to count from 0 to 59 minutes, 59 seconds and 9 tenths of a second.

An input (**ZERO**) reset the count. Another input (**start/stop**) is used to stop and restart the count.

An additional input (**TPARZ**) is used to memorize up to 4 partial times during counting; when the counting has been stop (by **start/stop**), **TPARZ** enables the transfer of the total time counted to a serial output (**OUT_T**) followed by the 4 partial times saved (if any is saved). A synchronism signal (**SYNC**) emits 1 pulse at the start of each time value transferred to **OUT_T**.

OUT_T values are 4-bits, BCD-coded, accounting to a total of 20 bits for each chronometer's value.

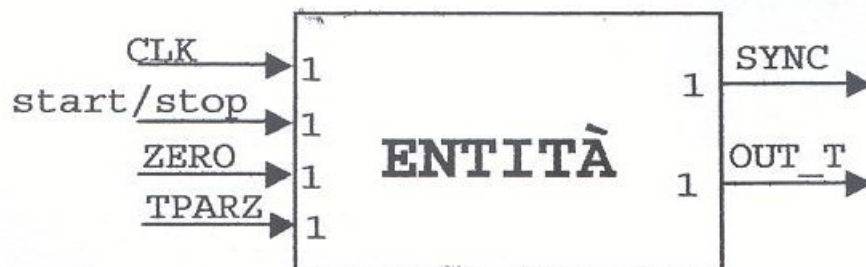Finally, **OUT_T** must be at high impedance in any other case.



```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.STD_LOGIC_ARITH.ALL;
4 use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6 entity Chrono is
7     port (CLK, START_STOP, ZERO, TPARZ: in std_logic;
8           SYNC, OUT_T: out std_logic);
9 end Chrono;
10
11 architecture Behavioral of Chrono is
12
13     --TIMES: to store the current time count and the partial time counts;
14     --time count is stored in the MSBs (20 bits);
15     --partial time counts are stored in the bits which come after.
16     signal TIMES: std_logic_vector (99 downto 0) := (others => '0');
17
18     --to count the number of sampled partial times
19     signal cntPT: integer range 0 to 5:=0;
20     signal state: std_logic:='0';
21     signal cnt: integer range 0 to 100:=0;
22
23     signal TENTHS: integer range 0 to 11:=0;    --Tenths of seconds.
24     signal M1, M2, S1, S2: integer range 0 to 11:=0; --Minutes and seconds.
25
26 begin
27
28     process (CLK, START_STOP, ZERO, TPARZ)
29     begin
30         if (ZERO = '1') then
31             --General reset:
32             TIMES <= (others => '0');
33             cntPT <= 0;
34             cnt <= 0;
35             TENTHS <= 0;
36             M1 <= 0;
37             M2 <= 0;
38             S1 <= 0;
39             S2 <= 0;
40
41         elsif (rising_edge (CLK)) then
42             if ((START_STOP = '0') and (state = '0')) then
43                 OUT_T <= 'Z';
44                 SYNC <= 'Z';
45
46             elsif (START_STOP = '1') then
47                 state <= '1'; --At least one time is counted.
48                 OUT_T <= 'Z'; --While the entity is counting, the output must be set to
49                 SYNC <= 'Z'; --high impedance.
50
51                 -----
52                 --Count (IT WORKS BUT I DON'T LIKE IT!):
53                 if (M2 < 6) then
54                     if (M1 < 10) then
55                         if (S2 < 6) then
56                             if (S1 < 10) then
57                                 if (TENTHS < 9) then TENTHS <= TENTHS + 1; end if;
58                                 if (TENTHS = 9) then
59                                     if (M2 /= 5) then TENTHS <= 0; end if;
60                                     if (S1 < 9) then S1 <= S1 + 1; end if;
61                                 end if;
62                             end if;
63                             if (S1 = 9 and TENTHS = 9) then
64                                 if (M2 /= 5) then S1 <= 0; end if;
65                                 if (S2 < 5) then S2 <= S2 + 1; end if;
66                             end if;
67                         end if;
68                         if (S2 = 5 and S1 = 9) then
69                             if (M2 /= 5) then S2 <= 0; end if;
70                             if (M1 < 9) then M1 <= M1 + 1; end if;
71                         end if;
72                     elsif (M1 = 9 and S2 = 5) then
73                         if (M2 /= 5) then M1 <= 0; end if;
74                         if (M2 < 5) then M2 <= M2 + 1; end if;
75                     end if;
76                 end if;
```

```

77
78 -----
79 --Partial times sampling:
80 if (TPARZ = '1') then
81     case cntPT is
82         --Partial time #1.
83         when 0 => TIMES(79 downto 60) <= conv_std_logic_vector(M2, 4) &
84             conv_std_logic_vector(M1, 4) &
85             conv_std_logic_vector(S2, 4) &
86             conv_std_logic_vector(S1, 4) &
87             conv_std_logic_vector(TENTHS, 4);
88             cntPT <= cntPT + 1;
89
90         --Partial time #2.
91         when 1 => TIMES(59 downto 40) <= conv_std_logic_vector(M2, 4) &
92             conv_std_logic_vector(M1, 4) &
93             conv_std_logic_vector(S2, 4) &
94             conv_std_logic_vector(S1, 4) &
95             conv_std_logic_vector(TENTHS, 4);
96             cntPT <= cntPT + 1;
97
98         --Partial time #3.
99         when 2 => TIMES(39 downto 20) <= conv_std_logic_vector(M2, 4) &
100             conv_std_logic_vector(M1, 4) &
101             conv_std_logic_vector(S2, 4) &
102             conv_std_logic_vector(S1, 4) &
103             conv_std_logic_vector(TENTHS, 4);
104             cntPT <= cntPT + 1;
105
106         --Partial time #4.
107         when 3 => TIMES(19 downto 0) <= conv_std_logic_vector(M2, 4) &
108             conv_std_logic_vector(M1, 4) &
109             conv_std_logic_vector(S2, 4) &
110             conv_std_logic_vector(S1, 4) &
111             conv_std_logic_vector(TENTHS, 4);
112             cntPT <= cntPT + 1;
113     when others => null;
114 end case;
115 end if;
116 -----
117
118 elsif ((START_STOP = '0') and (state = '1')) then
119 --Output bitstream generation:
120 if (cnt = 0) then
121     TIMES(99 downto 96) <= conv_std_logic_vector(M2, 4);
122     TIMES(95 downto 92) <= conv_std_logic_vector(M1, 4);
123     TIMES(91 downto 88) <= conv_std_logic_vector(S2, 4);
124     TIMES(87 downto 84) <= conv_std_logic_vector(S1, 4);
125     TIMES(83 downto 80) <= conv_std_logic_vector(TENTHS, 4);
126     cnt <= cnt + 1;
127 elsif ((cnt > 0) and (cnt <= 20+20*cntPT)) then
128     OUT_T <= TIMES(99);
129     TIMES <= TIMES(98 downto 0) & 'Z';
130     cnt <= cnt + 1;
131     case cnt is
132         when 1 => SYNC <= '1';
133         when 81 => SYNC <= '1';
134         when 61 => SYNC <= '1';
135         when 41 => SYNC <= '1';
136         when 21 => SYNC <= '1';
137         when others => SYNC <= '0';
138     end case;
139 elsif (cnt > 20+20*cntPT) then
140     OUT_T <= 'Z';
141     SYNC <= 'Z';
142 end if;
143
144 end if;
145
146 end if;
147 end process;
148
149 end Behavioral;

```