


14 January 2015

Create a clock-synchronous VHDL entity which starting from a reset analyses a serial input **DIN**.

If the first 8 bits are the 1-complement to the second 8 bits (example: 00011111 – 11100000), the output **BINGO**, which is normally 0, will emit an impulse for 1 clock cycle to signal the start of the serial output stream **DOUT**. Immediately after the pulse of **BINGO**, **DOUT** must emit the first 8 bits arriving to **DIN**.

If the 1-complement condition is not met, **BINGO** must still emit its impulse but **DOUT** must remain in high impedance state.

 When the **DISABLE** signal is active both outputs must be in high impedance state.



```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_ARITH.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6  --According to the description, the entity functioning seems to be one-shot.
7
8  entity PF is
9      port(CLK, RST, DIN, DIS: in std_logic;
10           BINGO, DOUT: out std_logic);
11 end PF;
12
13 architecture Behavioral of PF is
14
15     signal reg1: std_logic_vector (2 downto 0) := "ZZZ";
16     signal reg2: std_logic_vector (0 to 2) := "ZZZ";
17     signal regD, regB: std_logic := 'Z';
18     signal up1: bit := '0';
19     signal cnt: integer range 0 to 10 := 0;
20
21 begin
22
23     process (CLK, RST)
24     begin
25
26         --After a reset occurs, the entity begins to 'read' a serial input (DIN): 16 bits.
27         --NB: I've programmed just 6 bits in order to obtain a short testbench;
28         --in order to have a versatile solution, a constant can be used, but the
29         --following source code must be modified.
30         if (RST = '1') then
31             cnt <= 0;
32             reg1 <= "ZZZ";
33             reg2 <= "ZZZ";
34             up1 <= '0';
35
36         elsif (rising_edge(CLK)) then
37             --The first 8 bits (3) are forward-uploaded
38             --into a register, reg1:
39             if (cnt < 3) then
40                 reg1 <= reg1(1 downto 0) & DIN;
41                 regB <= '0';
42                 regD <= 'Z';
43                 cnt <= cnt + 1;
44             --The remaining 8 bits (3 or N) are reverse-uploaded into another
45             --register, reg2, in order to execute the subsequent comparison:
46             elsif (cnt > 2 and cnt < 5) then
47                 reg2 <= DIN & reg2(0 to 1);
48                 regB <= '0';
49                 regD <= 'Z';
50                 cnt <= cnt + 1;
51             --When the last bit is uploaded, the output signal 'BINGO'
52             --(normally at low level) goes high level for one clock period of time
53             --(regB is actually updated and then transferred to BINGO, if the entity is
54             --enabled):
55             elsif (cnt = 5) then
56                 reg2 <= DIN & reg2(0 to 1);
57                 regB <= '1';
58                 regD <= 'Z';
59                 cnt <= cnt + 1;
60
61
62
63
64
65
66
67
68
69
70
71
72
73
74
75
76
```

```
77 --If the first 8 (3) bits and the last 8 (3) ones are specular-like
78 --the first 8 (3) bits are tranferred to the serial output 'DOUT'
79 --otherwise DOUT is kept in high impedance state.
80 --NB: since reg1 is forward-uploaded, it must be tranferred to DOUT
81 --from the MSB to the LSB (*);
82 --NB: the signal 'upl' is used so that it's not required to control again
83 --whether reg1=reg2 or not (**);
84 --NB: reg1 and reg2 cannot be compared before this point, since reg2 is not
85 --completely uploaded yet.
86 elsif (cnt = 6) then
87     regB <= '0';
88     cnt <= cnt + 1;
89     if (reg1 = reg2) then
90         upl <= '1';
91         regD <= reg1(2); --(*)
92         reg1 <= reg1(1 downto 0) & 'Z';
93     else
94         regD <= 'Z';
95     end if;
96
97 --(**)
98 --NB: this 'elsif' body is necessary since as reg1 is tranferred to the output
99 --its content is updated and it can nomore be compared to reg2.
100 elsif (cnt = 7) then
101     regB <= '0';
102     if (upl = '1') then
103         regD <= reg1(2); --(*)
104         reg1 <= reg1(1 downto 0) & 'Z';
105     else
106         regD <= 'Z';
107     end if;
108 --NB: after the first DIN 8 (3) bits are tranferred to DOUT, the latter
109 --is kept in high impedance state until a new reset occurs (one-shot).
110 end if;
111 end if;
112 end process;
113
114 --If the entity is not disabled (DIS = 1), regD and regB are respectively
115 --tranferred to DOUT and BINGO.
116 DOUT <= regD when (DIS = '0') else 'Z';
117 BINGO <= regB when (DIS = '0') else 'Z';
118
119 end Behavioral;
```