


6 September 2006

Create a clock-synchronous VHDL entity with a serial input (**SDIN**) and a serial output (**OUTBCD**).

The entity must count the number of 1 in the input stream starting from the activation of the enable signal (**EN**) for 8 consecutive clock cycles. The count must be coded in BCD and transferred to the output during the next 4 clock cycles.

The entity must continue to count as described for as long as the entity is enabled. The output is in high impedance except when it transfers the output bitstream.

 Finally, the entity must have an asynchronous reset signal (**reset**).



```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_ARITH.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6  --serial input; serial output.
7  --The entity should count the occurrences of '1' in the input bitstream;
8  --it should start counting from an enabling signal
9  --(EN) commutation, for 8 clock periods of time and in the meantime output should
10 --be kept in high impedance state;
11 --the number of ones should be coded in 4 bits BCD format and later
12 --transferred to the output bitstream.
13 --The entity should continue its operation as EN is activated.
14 --Asynchronous should be performed.
15
16 entity BCD is
17     port(RST, CLK, SIN, EN: in std_logic;
18          SOUT: out std_logic);
19 end BCD;
20
21 architecture Behavioral of BCD is
22     signal cnt: integer range 0 to 15:=0;
23     signal reg: std_logic_vector (3 downto 0):="0000";
24     --NB: since the package "unsigned" is used, reg can be simply
25     --incremented; 4 bits of reg can be manipulated as an unsigned
26     --value.
27 begin
28
29 process (EN, RST, CLK)
30 begin
31     --1) RST=1: general reset;
32     if (RST = '1') then
33         cnt <= 0;
34         reg <= "0000";
35         SOUT <= 'Z';
36     --2) RST=0:
37     elsif (rising_edge(CLK)) then
38         if (cnt < 8) then
39             --3)
40             --(8 CLK periods of time)
41             --EN=0: doesn't count;
42             --EN=1 counts.
43             --cnt is incremented anyway.
44             --SOUT is kept in high impedance state.
45             if (EN = '1' and SIN = '1') then
46                 reg <= reg + 1;
47             end if;
48             SOUT <= 'Z';
49             cnt <= cnt + 1;
50             --4) reg is transferred to SOUT from LSB to MSB (4 CLK periods of time).
51             elsif (cnt > 7 and cnt < 11) then
52                 SOUT <= reg (0);
53                 reg <= 'Z' & reg (3 downto 1);
54                 cnt <= cnt + 1;
55             --5) by the time the MSB is transferred to SOUT, cnt and reg should be
56             --reset to 0 and 0000 in order to start a new count.
57             elsif (cnt = 11) then
58                 SOUT <= reg (0);
59                 reg <= "0000";
60                 cnt <= 0;
61             end if;
62         end if;
63     end process;
64
65 end Behavioral;
```