 


9 November 2006

Create a clock-synchronous VHDL entity with two 4-bits inputs (**DATA_X**, **DATA_Y**) and one serial output (**OUTPIXEL**).


The entity must pilot a 16x16 display as showed in the picture:



After receiving a pair of values at the inputs, the output must scan through the display, one pixel per clock cycle, starting from the top left pixel and proceed as shown in the picture. The output must be equal to 1 only at the position specified by the input signals.

Avoid the accumulation of data inside the entity.

 When the entity is not enabled, the output must be set to high impedance.



```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity disdri is
    Port ( clk : in std_logic;
          en : in std_logic;
          datax : in std_logic_vector(3 downto 0);
          datay : in std_logic_vector(3 downto 0);
          outpixel : out std_logic);
end disdri;

architecture Behavioral of disdri is
    signal cont: INTEGER :=0;
    signal pixone: std_logic_vector(7 downto 0);
    signal regx : std_logic_vector(3 downto 0);
    signal regy : std_logic_vector(3 downto 0);

begin

    p1:process(clk)
    begin
        if en='1' then
            if rising_edge(clk) then
                if cont=0 then
                    regx<=datax;
                    regy<=datay;
                    outpixel<='0';
                    cont<= cont +1;
                elsif cont >0 and cont <255 then
                    cont<= cont +1;
                    if cont=conv_integer(pixone) then
                        outpixel<='1';
                    else outpixel<='0';
                    end if;
                elsif cont=255 then
                    cont<=0;
                end if;
            end if;
        elsif en='0' then
            outpixel<='Z';
        end if;
    end process;

    p2:process(clk)
    begin
        if rising_edge(clk) then
            if (regy and "0001") = "0000" then
                pixone <= regy & regx;
            else
                pixone <= regy & not(regx);
            end if;
        end if;
    end process;
end Behavioral;

```