

11 July 2006

Create a VHDL entity synchronous to a clock signal with 2 4-bits inputs:

**A** (a3, a2, a1, a0)

**B** (b3, b2, b1, b0)


and 2 serial outputs: **out1** and **out2**

The entity must produce the output as described in the table below, depending on the value of a selection signal (**sel**):

<b>sel</b>	<b>out1</b>	<b>out2</b>
0	High z	High z
1	a3 a2 a1 a0	b3 b2 b1 b0
2	b0 b1 b2 b3	a0 a1 a2 a3
3	b3 a0 b2 a1 b1 a2 b0 a3	a3 b0 a2 b1 a1 b2 a0 b3

Avoid the accumulation of data inside the entity.

 The entity must provide an asynchronous reset signal (**reset**) which reset the state of the entity and at the same time set the output to high impedance.



```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_ARITH.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6
7  entity PF4 is
8      port(CLK, RST: in std_logic;
9           sel: in std_logic_vector (1 downto 0);
10          A, B: in std_logic_vector (3 downto 0);
11          out1, out2: out std_logic);
12 end PF4;
13
14
15 architecture Behavioral of PF4 is
16
17     signal cnt: integer range 0 to 15:=0;
18     signal reginA: std_logic_vector (3 downto 0):=(others => 'Z');
19     signal reginB: std_logic_vector (3 downto 0):=(others => 'Z');
20     signal regin1: std_logic_vector (7 downto 0):=(others => 'Z');
21     signal regin2: std_logic_vector (7 downto 0):=(others => 'Z');
22     signal regsel: std_logic_vector (1 downto 0):="ZZ";
23
24     begin
25
26         process (CLK, RST)
27             begin
28
29                 if (RST='1') then
30                     cnt <= 0;
31                     reginA <= (others => 'Z');
32                     reginB <= (others => 'Z');
33                     regsel <= "ZZ";
34                     out1 <= 'Z';
35                     out2 <= 'Z';
36
37                 elsif rising_edge(CLK) then
38                     if (cnt=0) then
39                         reginA <= A;
40                         reginB <= B;
41                         regsel <= sel;
42
43                         regin1(7) <= B(3);
44                         regin1(6) <= A(0);
45                         regin1(5) <= B(2);
46                         regin1(4) <= A(1);
47                         regin1(3) <= B(1);
48                         regin1(2) <= A(2);
49                         regin1(1) <= B(0);
50                         regin1(0) <= A(3);
51
52                         regin2(7) <= A(3);
53                         regin2(6) <= B(0);
54                         regin2(5) <= A(2);
55                         regin2(4) <= B(1);
56                         regin2(3) <= A(1);
57                         regin2(2) <= B(2);
58                         regin2(1) <= A(0);
59                         regin2(0) <= B(3);
60
61                         out1 <= 'Z';
62                         out2 <= 'Z';
63                         cnt <= cnt + 1;
64
65
66
67
68
69
70
71
72
73
74
75
76
```

```
77         elsif (cnt > 0) then
78             case regsel is
79                 when "00" => out1 <= 'Z';
80                             out2 <= 'Z';
81
82                 when "01" => if (cnt <5) then
83                             out1 <= reginA(3);
84                             out2 <= reginB(3);
85                             reginA <= reginA(2 downto 0) & 'Z';
86                             reginB <= reginB(2 downto 0) & 'Z';
87                             cnt <= cnt + 1;
88                             elsif (cnt >= 5) then
89                                 out1 <= 'Z';
90                                 out2 <= 'Z';
91                             end if;
92
93                 when "10" => if (cnt <5) then
94                             out1 <= reginB(0);
95                             out2 <= reginA(0);
96                             reginA <= 'Z' & reginA(3 downto 1);
97                             reginB <= 'Z' & reginB(3 downto 1);
98                             cnt <= cnt + 1;
99                             elsif (cnt >= 5) then
100                                 out1 <= 'Z';
101                                 out2 <= 'Z';
102                             end if;
103
104                 when "11" => if (cnt <9) then
105                             out1 <= regin1(7);
106                             out2 <= regin2 (7);
107                             regin1 <= regin1(6 downto 0) & 'Z';
108                             regin2 <= regin2(6 downto 0) & 'Z';
109                             cnt <= cnt + 1;
110                             elsif (cnt >= 8) then
111                                 out1 <= 'Z';
112                                 out2 <= 'Z';
113                             end if;
114
115                 when others => out1 <= 'Z';
116                             out2 <= 'Z';
117
118             end case;
119
120         end if;
121
122     end if;
123
124 end process;
125
126 end Behavioral;
```

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_ARITH.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6  --data input: 2 parallel 4 bits; 2 parallel bits (A and B);
7  --selection input: 2 parallel bits (SEL);
8  --output: 2 serial signals, out1 and out2 (bitstream process is explained later).
9
10 entity P_to_S is
11     port(CLK, RST: in std_logic;
12          SEL: in std_logic_vector(1 downto 0):="00";
13          A, B: in std_logic_vector(3 downto 0):="ZZZZ";
14          out1, out2: out std_logic);
15 end P_to_S;
16
17 architecture Behavioral of P_to_S is
18     signal cnt: integer range 0 to 10:=0;
19     signal regA, regB: std_logic_vector(3 downto 0):="ZZZZ";
20     signal regSEL: std_logic_vector(1 downto 0):="ZZ";
21 begin
22
23     process (CLK, RST)
24     begin
25         if (RST = '1') then
26             cnt <= 0;
27             regA <= "ZZZZ";
28             regB <= "ZZZZ";
29             out1 <= 'Z';
30             out2 <= 'Z';
31         elsif (rising_edge(CLK)) then
32             --1) upload A and B into regA and regB (cnt=0) and out1,2='Z'
33             --at the same time SEL input can be controlled; SEL might change
34             --while output bitstream is processed, thus the content of SEL
35             --is stored into regSEL just at this point;
36             if (cnt = 0) then
37                 regSEL <= SEL;
38                 regA <= A;
39                 regB <= B;
40                 out1 <= 'Z';
41                 out2 <= 'Z';
42                 cnt <= cnt + 1;
43             --2) at this point, regSEL is ready and its content can be controlled
44             --NB: if SEL=00, out1 and out2 are kept in high impedance state indefinitely;
45             --otherwise, after the output bitstreams end, the entity makes a new selection
46             --in other words, a new occurrence of SEL is stored into regSEL.
47             elsif (cnt > 0) then
48                 case regSEL is
49                     --regSEL=00: output in high impedance state until a reset occurs;
50                     when "00" => out1 <= 'Z';
51                                     out2 <= 'Z';
52                     --regSEL=01: out1=a3...10; out2=b3...b0.
53                     when "01" => out1 <= regA(3);
54                                     regA <= regA(2 downto 0) & 'Z';
55                                     out2 <= regB(3);
56                                     regB <= regB(2 downto 0) & 'Z';
57                                     if (cnt = 4) then
58                                         cnt <= 0;
59                                     else
60                                         cnt <= cnt + 1;
61                                     end if;
62                     --regSEL=10: out1=b0...b3; out2=a0...a3
63                     when "10" => out1 <= regB(0);
64                                     regB <= 'Z' & regB(3 downto 1);
65                                     out2 <= regA(0);
66                                     regA <= 'Z' & regA(3 downto 1);
67                                     if (cnt = 4) then
68                                         cnt <= 0;
69                                     else
70                                         cnt <= cnt + 1;
71                                     end if;
72
73
74
75
76

```

```
77      --regSEL=11: out1: b3a0b2a1b1a2b0a3; out2: a3b0a2b1a1b2a0b3
78      when "11" => if (cnt = 1) then
79          out1 <= regB(3);
80          out2 <= regA(3);
81          cnt <= cnt + 1;
82      elsif (cnt = 2) then
83          out1 <= regA(0);
84          out2 <= regB(0);
85          cnt <= cnt + 1;
86      elsif (cnt = 3) then
87          out1 <= regB(2);
88          out2 <= regA(2);
89          cnt <= cnt + 1;
90      elsif (cnt = 4) then
91          out1 <= regA(1);
92          out2 <= regB(1);
93          cnt <= cnt + 1;
94      elsif (cnt = 5) then
95          out1 <= regB(1);
96          out2 <= regA(1);
97          cnt <= cnt + 1;
98      elsif (cnt = 6) then
99          out1 <= regA(2);
100         out2 <= regB(2);
101         cnt <= cnt + 1;
102     elsif (cnt = 7) then
103         out1 <= regB(0);
104         out2 <= regA(0);
105         cnt <= cnt + 1;
106     elsif (cnt = 8) then
107         out1 <= regA(3);
108         out2 <= regB(3);
109         cnt <= 0;
110     end if;
111     when others => cnt <= 0; --an error occurred in this case
112                          --hopefully this won't happen.
113 end case;
114 end if;
115 end if;
116
117 end process;
118
119 end Behavioral;
120
```