


19 September 2008

Create a clock-synchronous VHDL entity which splits input serial data (**DIN**) into 3 serial output streams.

Starting from a reset, a selection 2-bits signal (**SEL**) is sampled. This signal determines which output starts to stream while the other outputs stay at high impedance.

The input signal **ROTATE** determines a change in the active output following an order decided by the student.

 The **ENABLE** signal deactivates the outputs and keep them at high impedance while the entity internal function is not affected.



```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_ARITH.ALL;
4  use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6  entity selection is
7      port (CLK, RST, EN, DIN, ROT: in std_logic;
8            SEL: in std_logic_vector (1 downto 0);
9            OUT1, OUT2, OUT3: out std_logic);
10 end selection;
11
12 architecture Behavioral of selection is
13
14     signal REG: std_logic_vector (1 downto 0) := "00";
15     signal reg1, reg2, reg3: std_logic := 'Z';
16
17     begin
18
19         process (CLK, RST)
20         begin
21             if (RST = '1') then
22                 REG <= SEL;
23                 OUT1 <= 'Z';
24                 OUT2 <= 'Z';
25                 OUT3 <= 'Z';
26             elsif rising_edge (CLK) then
27                 if (REG = "00") then
28                     REG <= SEL;
29                     OUT1 <= 'Z';
30                     OUT2 <= 'Z';
31                     OUT3 <= 'Z';
32                 elsif (REG = "01") then
33                     reg1 <= DIN;
34                     reg2 <= 'Z';
35                     reg3 <= 'Z';
36                     if (ROT = '1') then
37                         REG <= "10";
38                     end if;
39                 elsif (REG = "10") then
40                     reg1 <= 'Z';
41                     reg2 <= DIN;
42                     reg3 <= 'Z';
43                     if (ROT = '1') then
44                         REG <= "11";
45                     end if;
46                 elsif (REG = "11") then
47                     reg1 <= 'Z';
48                     reg2 <= 'Z';
49                     reg3 <= DIN;
50                     if (ROT = '1') then
51                         REG <= "01";
52                     end if;
53                 end if;
54             end if;
55         end process;
56
57         OUT1 <= reg1 when (EN = '1') else 'Z';
58         OUT2 <= reg2 when (EN = '1') else 'Z';
59         OUT3 <= reg3 when (EN = '1') else 'Z';
60
61     end Behavioral;
```